

[← Go Back](#)

Hardware

UNO R3



Tutorials

[Analog Input](#)[Analog Read Serial](#)[Blink](#)[Digital Read Serial](#)[Arduino UNO Board
Anatomy](#)[Getting Started with
Arduino UNO R3](#)[Overview of the Arduino
UNO Components](#)[Controlling PWM Output
with a Potentiometer via
MATLAB®](#)[Home](#) / [Hardware](#) / [UNO R3](#) /[Blink](#)

ON THIS PAGE

Hardware Required

[Circuit](#)[Schematic](#)[Code](#)[Learn more](#)

Blink

Turn an LED on and off every second.

Last revision • 10/02/2024

This example shows the simplest thing you can do with an Arduino to see physical output: it blinks the on-board LED.

Hardware Required

Arduino Board

optional

LED

220 ohm resistor

Circuit

This example uses the built-in LED that most Arduino boards have. This LED is connected to a digital pin and its number may vary from board type to board type. To make your life easier, we have a constant that is specified in every board descriptor file. This constant is `LED_BUILTIN` and allows you to control the built-in LED easily. Here is

[Help](#)

the constant and the digital pin.

D13 - 101

D13 - Due

D1 - Gemma

D13 - Intel Edison

D13 - Intel Galileo
Gen2

D13 - Leonardo and
Micro

D13 - LilyPad

D13 - LilyPad USB

D13 - MEGA2560

D13 - Mini

D6 - MKR1000

D13 - Nano

D13 - Pro

D13 - Pro Mini

D13 - UNO

D13 - Yún


D13 - Zero

If you want to light an external LED with this sketch, you need to build this circuit, where you connect one end of the resistor to the digital pin correspondent to the *LED_BUILTIN* constant.


Connect the long leg of the LED (the positive leg, called the anode) to the other end

negative leg, called the cathode) to the GND. In the diagram below we show an UNO board that has D13 as the LED_BUILTIN value.

The resistor is essential for safe operation as it limits the current flowing through the LED, preventing damage to both the LED and the Arduino's output pin. You can choose the resistor value based on the desired current using Ohm's Law ($V = IR$) where V is the voltage of your board (5V or 3.3V) minus the forward voltage for the LED you are using (typical for red would be 1.8 to 2.2 volts). In this case, using a 220-ohm resistor with an Arduino UNO R3 (a 5V board) limits the current to a safe level for both the LED and the Arduino pin. Adjusting the resistor value allows you to control the LED's brightness while ensuring safe operation. For 5V boards you can expect the LED to be visible to a resistor value of up to 1K Ohm.

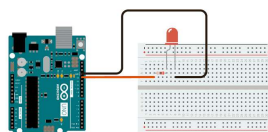

Schematic

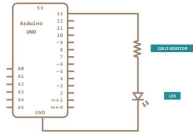

Code

After you build the circuit plug your Arduino board into your computer, start the Arduino Software (IDE) and enter the code below. You may also load it from the menu File/Examples/01.Basics/Blink . The first thing you do is to initialize LED_BUILTIN pin as an output pin with the line

```
pinMode(LED_BUILTIN,
OUTPUT);
```

In the main loop, you turn the LED on with the line:

```
digitalWrite(LED_BUILTIN
, HIGH);
```

This supplies 5 volts to the LED anode. That creates a voltage difference across the pins of the LED, and lights it up. Then you turn it off with the line:

```
digitalWrite(LED_BUILTIN
, LOW);
```

That takes the LED_BUILTIN pin back to 0 volts, and turns the LED off. In between the on and the off, you want enough time for a person to see the change, so the `delay()` commands tell the

milliseconds, or one second.

When you use the `delay()` command, nothing else happens for that amount of time. Once you've understood the basic examples, check out the [BlinkWithoutDelay](#) example to learn how to create a delay while doing other things.

Once you've understood this example, check out the [DigitalReadSerial](#) example to learn how read a switch connected to the board.

```
1  /*
2  Blink
3
4  Turns an
  LED on for
  one second,
  then off
  for one
  second,
  repeatedly.

5
6  Most
  Arduinos
  have an on-
  board LED
  you can
  control. On
  the UNO,
  MEGA and
  ZERO
7  it is
  attached to
  digital pin
  13, on
  MKR1000 on
  pin 6.
  LED_BUILTIN
  is set to
8  the
  correct LED
  pin
  independent
  of which
  board is
  used.

9  If you
  want to
  know what
  pin the on-
```

See Also

Learn more

You can find more basic tutorials in the [built-in examples](#) section.

You can also explore the [language reference](#), a detailed collection of the Arduino programming

Last revision 2015/07/28 by
SM

Suggest changes	Need support?	License
The content on docs.arduino.cc is facilitated through a public GitHub repository. If you see anything wrong, you can edit this page here.	Help Center Ask the Arduino Forum Discover Arduino Discord	The Arduino documentation is licensed under the Creative Commons Attribution Share Alike 4.0 license

Was this article helpful?

